


Name: Parity Generator and Checker

Objective: In this experiment, we have to implement an Even parity Generator and an Even parity checker, we have to use XOR gate for this experiment.


Required Components: 1. AT-700 portable Analog/Digital Laboratory
2. 7486

Experimental Setup:

Generator:

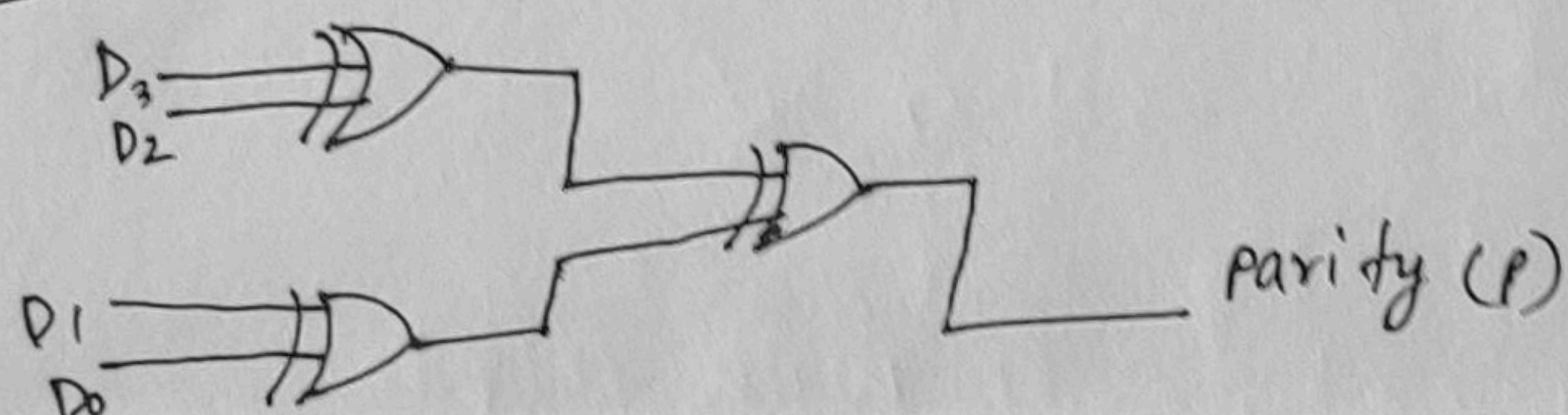

Checker:

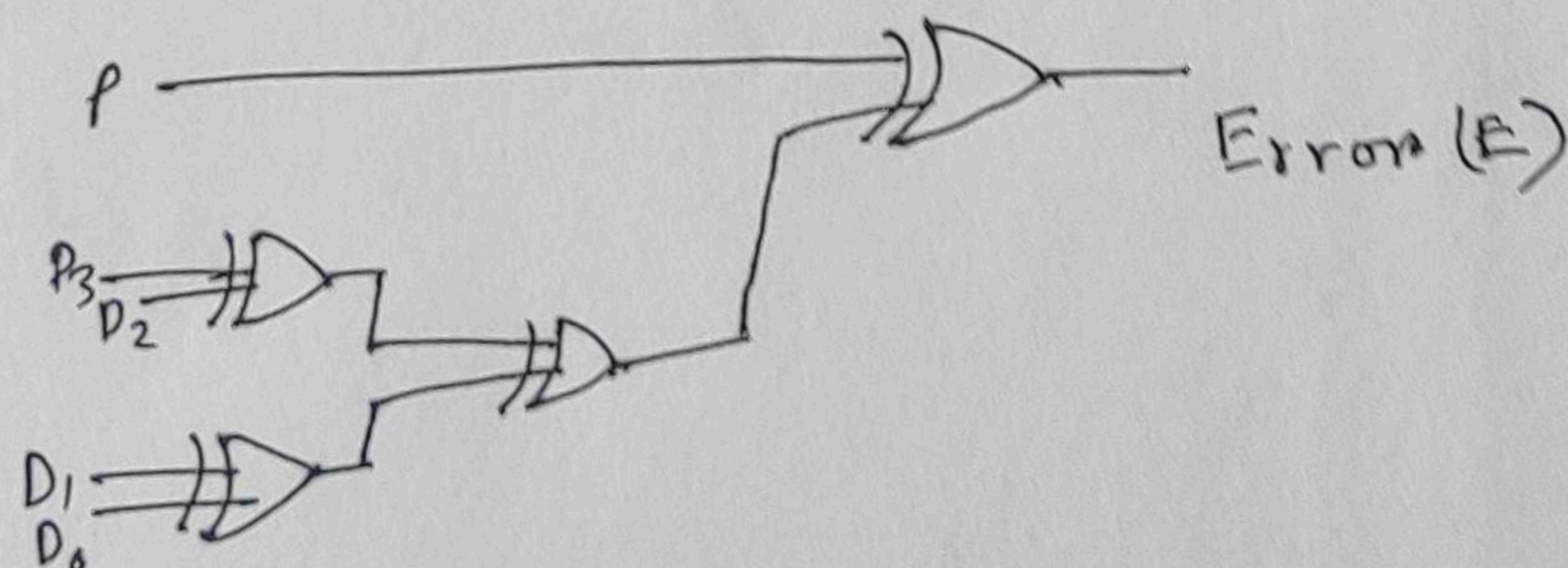

D_3 D_2 D_1 D_0 output

0 1 1 1 1

1 0 0 1 0

0 0 0 0 0

0 1 0 0 1

D_3 D_2 D_1 D_0 output

1 0 1 0 0 (no error)

1 1 1 0 0 (no error)

1 1 1 1 1 (error)

0 0 0 0 1 (error)

Discussion: In this experiment, we are ~~checking~~
~~the parity~~ creating an even parity generator and
an even parity checker, using XOR gates. In case of
even parity generator, the generator successfully generates
the parity, resulting if the number of 1's is even, it generates
0 as output, and if the number of 1's is odd, it generates
1 as output.

In case of parity checker, we are checking whether the
result of our experiment matches theoretically and practically.
If the result matches, we are indicating it with 0 (no-
error) and if the result does not match, we are
indicating it with 1 (error).