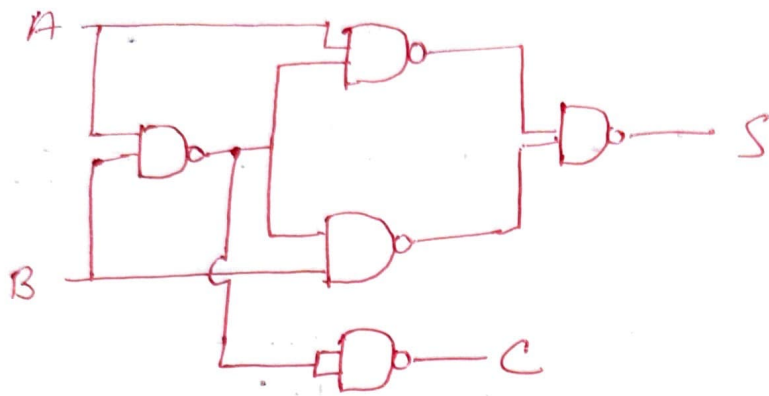


A-3 Solution


1) Half Adder using NAND




2) 2's complement to binary

Truth Table

A_2	A_1	A_0	A_2	A_1	A_0
0	0	0	0	0	0
0	0	1	1	1	1
0	1	0	1	1	0
0	1	1	1	0	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	0	0	1

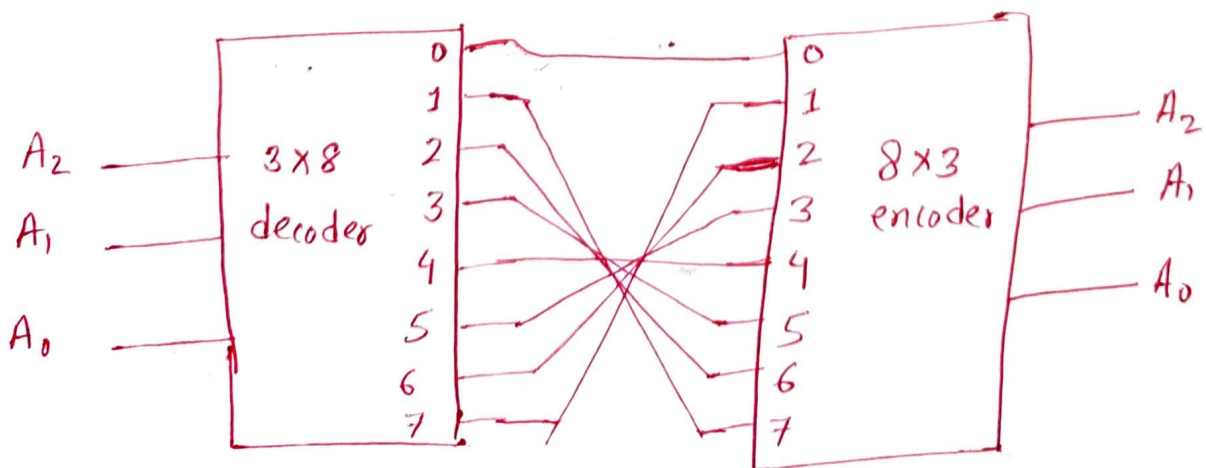


3) 14-person voting system

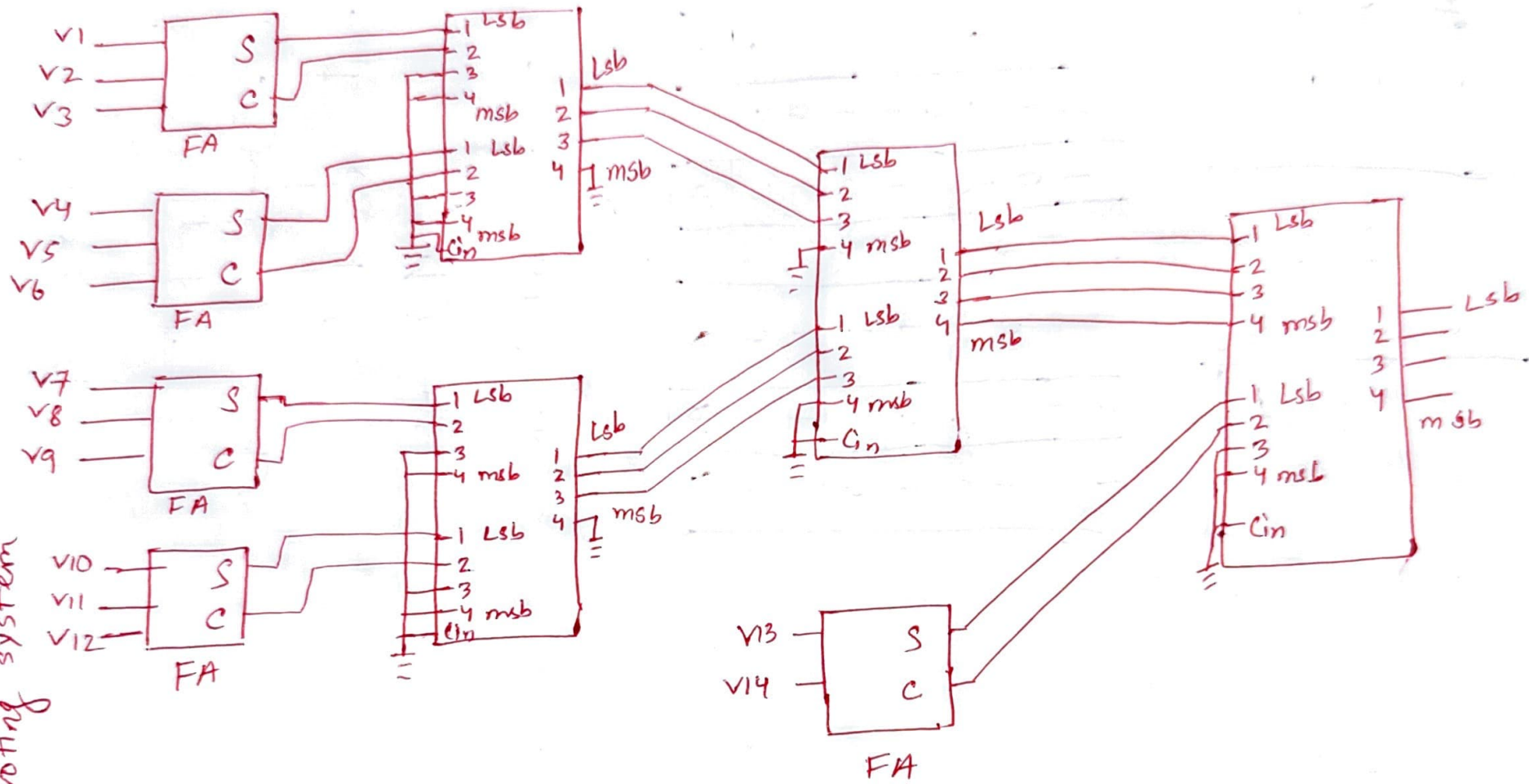


4) $F(A, B, C, D) = \sum (0, 1, 2, 4, 5, 7, 11, 12, 14)$

a) 16:1 Mux

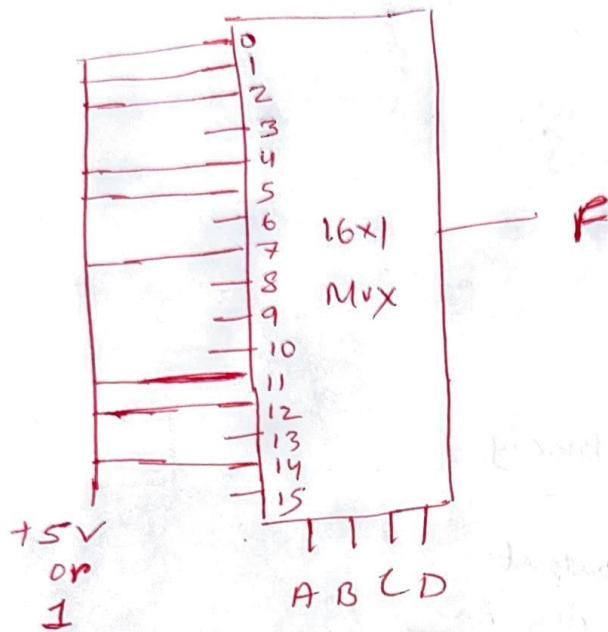

b) Single 8:1 Mux

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
A'	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	A'	A'	A'	A	1	A'	A	A'

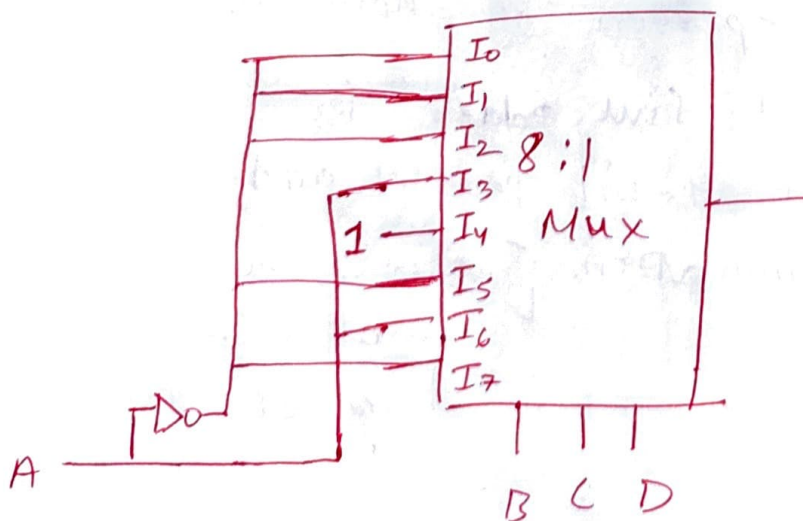

Must use external gates for A' .

1c) single 4:1 Mux.


	I_0	I_1	I_2	I_3
$A'B'$	0	1	2	3
$A'B$	4	5	6	7
$A'B'$	8	9	10	11
AB	12	13	14	15

$$\begin{aligned}
 I_0 &= A'B' + A'B + AB \\
 &= A'(B' + B) + AB \\
 &= A' + AB \\
 &= (A' + A)(A' + B) \\
 &= A' + B
 \end{aligned}$$

$$\begin{aligned}
 I_1 &= A'B' + A'B \\
 &= A'(B' + B) \\
 &= A'
 \end{aligned}$$


$$\begin{aligned}
 I_2 &= A'B' + AB \\
 &= A \odot B
 \end{aligned}$$
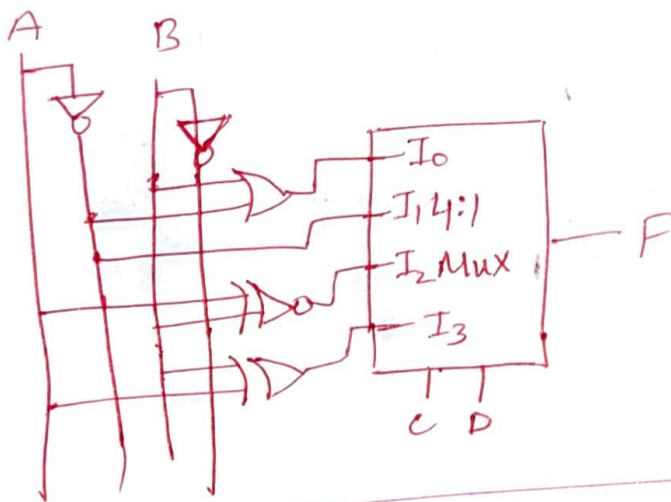
$$\begin{aligned}
 I_3 &= A'B + AB' \\
 &= A \oplus B
 \end{aligned}$$



5) $F(A, B, C, D, E) = \Sigma(0, 1, 5, 15, 24, 25, 27)$

a) 4x16 decoder only

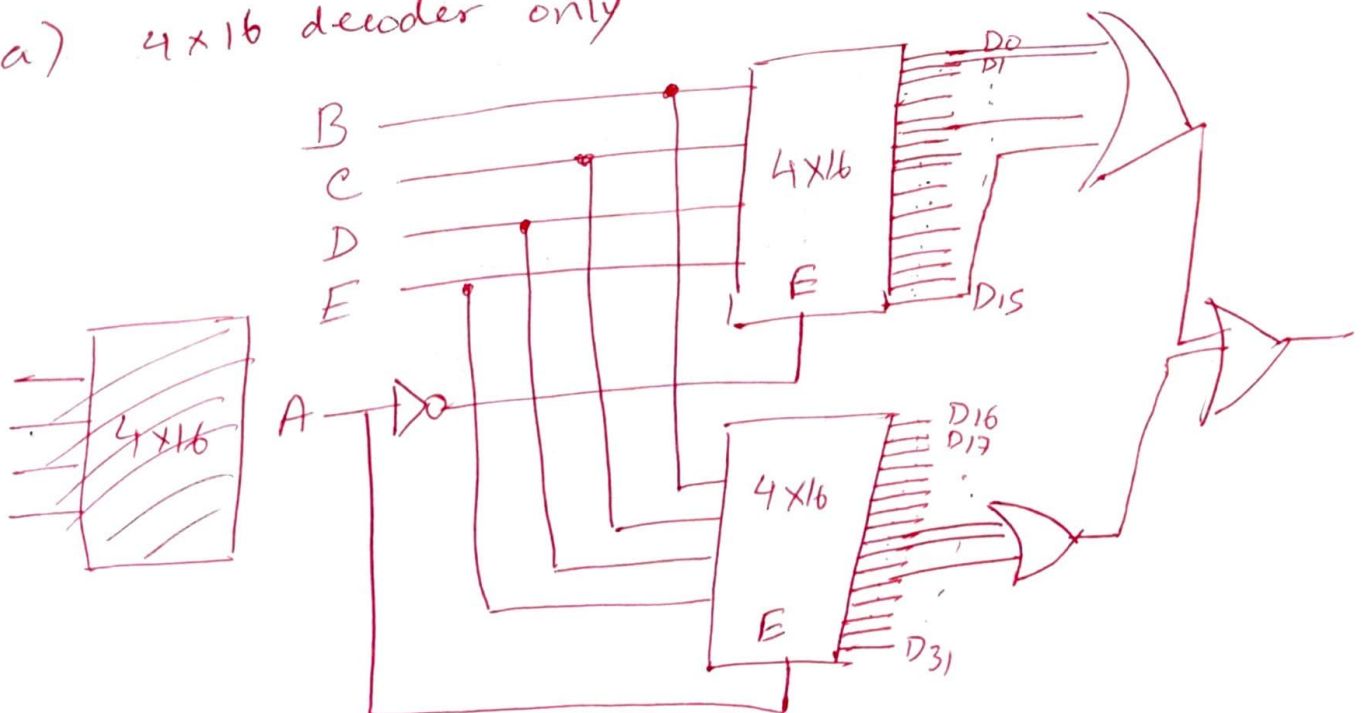

5b) 2x4 decoders only

