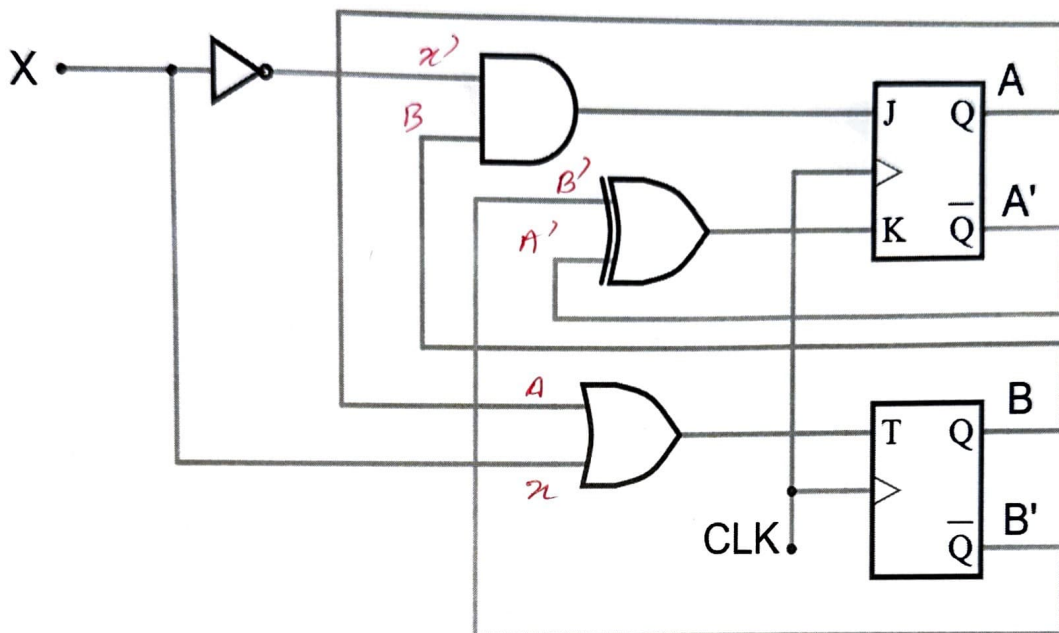


Name:

ID:

Section:

Question 1 [CO3]: Draw the state diagram for the given circuit.



$$JA = Bx'$$

$$KA = A' \oplus B'$$

$$TB = A + x$$

State Table

A	B	x	JA	KA	TB	A+	B+
0	0	0	0	0	0	0	0
0	0	1	0	0	1	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	0
1	0	0	0	1	1	0	1
1	0	1	0	1	1	0	1
1	1	0	1	0	1	1	0
1	1	1	0	0	1	1	0

State Diagram

