



Inspiring Excellence

CSE260: Digital Logic Design

Spring 2025

Quiz - 04

Duration: 30 Minutes


B

Name:

ID:

Section:

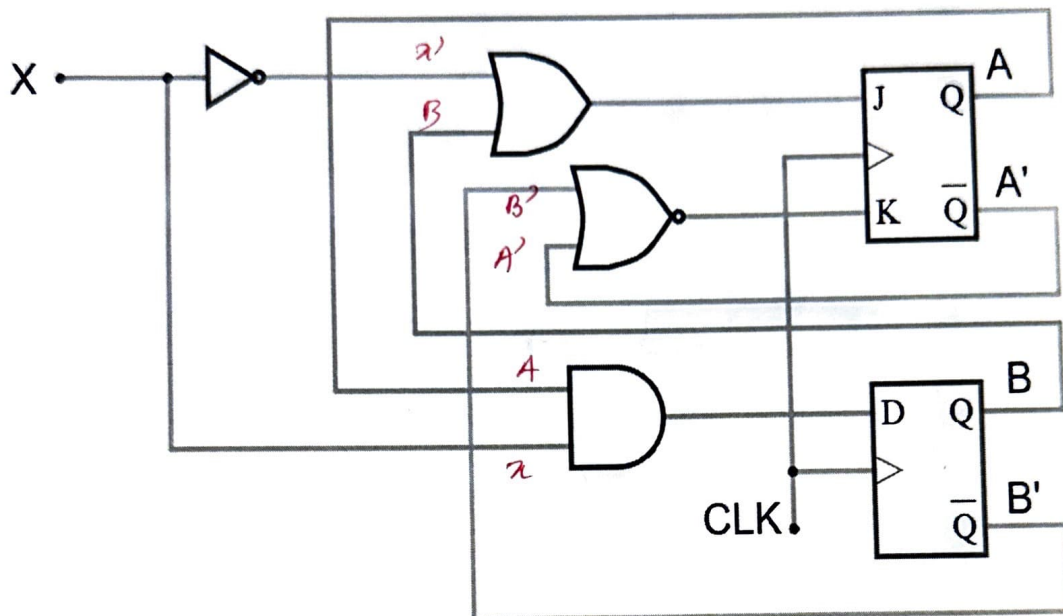Question 1 [CO3]: Draw the state diagram for the given circuit.



$$JA = B + X'$$

$$KA = \overline{(A' + B')} = A \cdot B$$

$$DB = A \cdot X$$

State Table

A	B	X	JA	KA	DB	A+	B+
0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0
0	1	0	1	0	0	1	0
0	1	1	1	0	0	1	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	1	1
1	1	0	1	1	0	0	0
1	1	1	1	1	1	0	1

State Diagram

