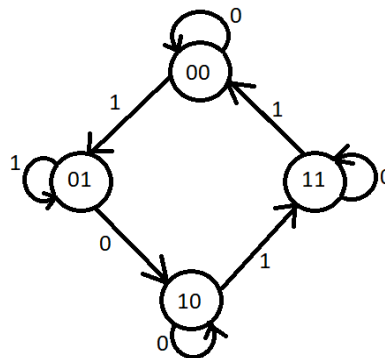


CSE260 Assignment - 4
Deadline - 11th May, 11:59 PM
Marks : 10

Assignment must be handwritten. Submit Soft Copy PDF in Google Form


Question 1: (5 Marks)

Given the state diagram, get the sequential circuit using SR flip-flop. Show all necessary tables.



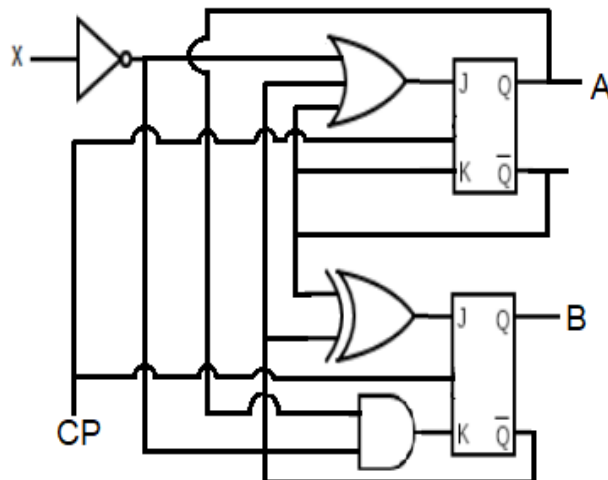Question 2: (5 Marks)

Draw the state diagram for the given circuit.



Ungraded Problems: Only for Practice, NO NEED TO SUBMIT

Question 1

Implement the following counter using T flip flop

CSE110 -> CSE111 -> CSE220 -> CSE221 -> CSE331 -> CSE221 -> CSE321 -> CSE110

Question 2

Implement 3 bits up/down counter using D flip flop

Question 3

3->4->6->10->12->13->15->3

- Implement the given counter using JK flip-flop.
- Implement the given counter using T flip-flop.

NB: For states not given in question, please move to the initial state as per question.

Question 4

Implement the following counter using D flip flop

A -> B -> C -> B -> D -> B -> A

Question 5

What is the total capacity of a $2^{32} \times 16$ memory?

Question 6

Draw the block diagram for a 1024x16 RAM.

Question 7

Given the state diagram as follows, get the sequential circuit using

- SR flipflop.
- JK flipflop.

