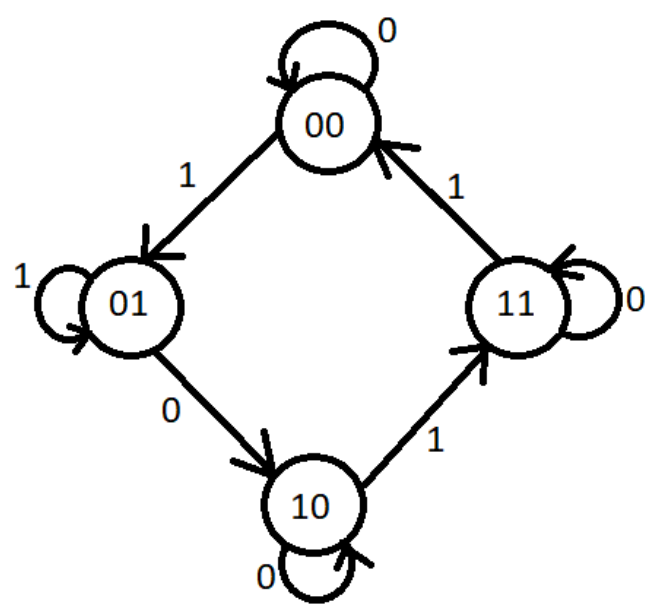





STATE TABLE


A	B	X	A+	B+	SA	RA	SB	RB
0	0	0	0	0	0	x	0	x
0	0	1	0	1	0	x	1	0
0	1	0	1	0	1	0	0	1
0	1	1	0	1	0	x	x	0
1	0	0	1	0	x	0	0	x
1	0	1	1	1	x	0	1	0
1	1	0	1	1	x	0	x	0
1	1	1	0	0	0	1	0	1

Q	Q+	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


SR Flip-flop

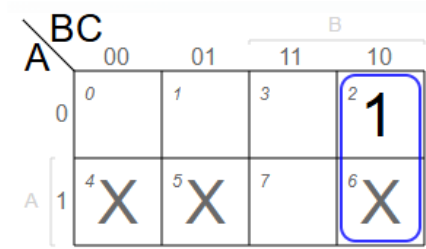


$SA = BX'$

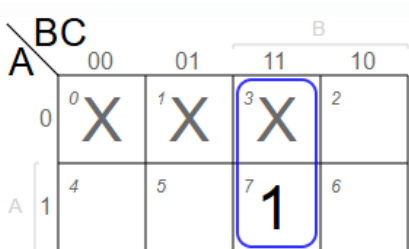


$RA = BX$

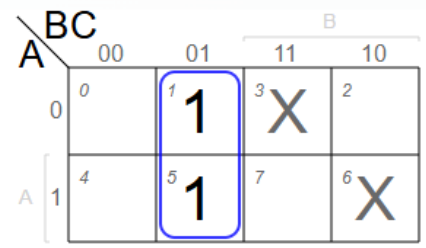


$SB = B'X$

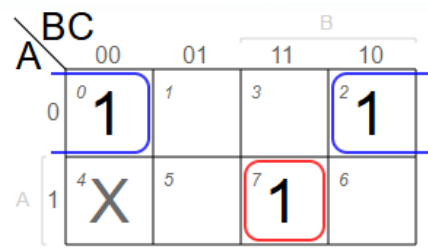

$RB = A'X' + ABX$

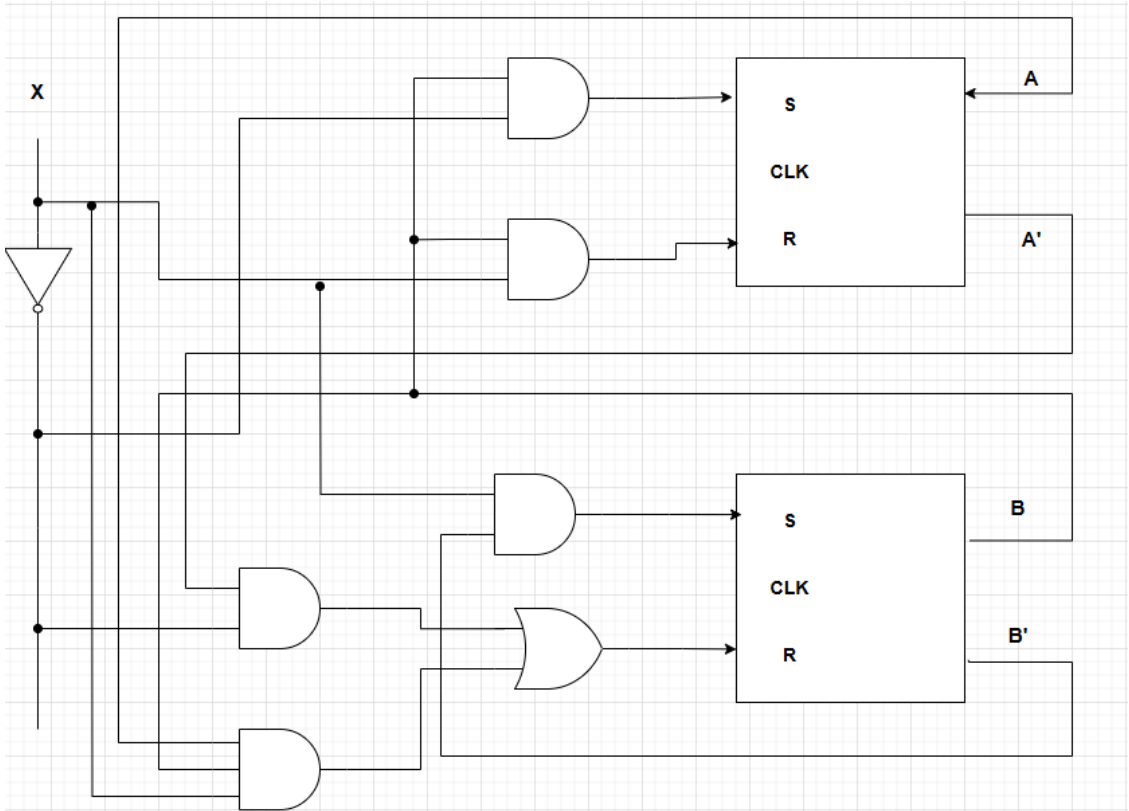

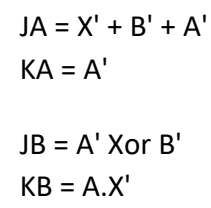

A	B	X	A+	B+	JA	KA	JB	KB
0	0	0	1	0	1	1	0	0
0	0	1	1	0	1	1	0	0
0	1	0	1	1	1	1	1	0
0	1	1	1	1	1	1	1	0
1	0	0	1	1	1	0	1	1
1	0	1	1	1	1	0	1	0
1	1	0	1	0	1	0	0	1
1	1	1	1	1	0	0	0	0

